

Q. No	Topic/Questions	Page No
Unit - 9C (GATES)		
1.	a) What are logic Gates? Name various types of Gates b) Discuss symbol, Boolean expression (Equation) and Truth Table of different Gates	9/24
2.	Discuss Symbol, Boolean expression and Truth Table of Gates.	9/24
3.	De Morgan's first theorem	9/27
4.	De Morgan's second theorem	9/27
5.	Problems Related to Logic Gates	9/28
Important Board Questions		
1.	What is Integrated circuit?	9/37
2.	Make AND gate by using NOR gate	9/38
3.	Make AND gate by using NAND gate.	9/39
4.	Make OR gate by using NAND gate.	9/39
5.	Sketch the output y from a NAND gate having inputs A and B given below.	9/40
6.	Sketch the output y from a NOR gate having inputs A and B as given in Fig.	9/40

Unit - 9C (GATES)

Q1. a) What are logic Gates? Name various types of Gates.

b) Discuss symbol, Boolean expression (Equation) and Truth Table of different Gates.

Ans: a) Logic gates:- A digital circuit which either allows a signal to pass through or stops it, when some logical conditions are satisfied called logic gates.

b) Various types of gates are:-

- a) NOT Gate
- b) OR Gate
- c) AND Gate
- d) NOR Gate
- e) NAND Gate
- f) XOR Gate
- g) X - NOR Gate

* NOR Gate and NAND Gate are called digital building block Gates.

Q2. Discuss Symbol, Boolean expression and Truth Table of Gates.

Ans. a) NOT Gate

Step1 Symbol



Step2 Equation or Boolean Expression


$Y = \bar{A}$ (Read Y is compliment of A)

Step3 Truth Table

A	Y
0	1
1	0

b) OR Gate

Step1 Symbol

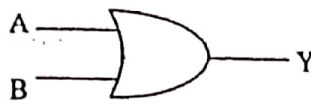

Step2 Equation

$Y = A + B$ [Read A ored with B]

Step3 Truth Table

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1




+2 / Unit 9C / Q1 Types of Gates



+2 / Unit 9C / Symbol Boolean Expression Truth Table Theorems Numericals

c) AND Gate

Step1 Symbol

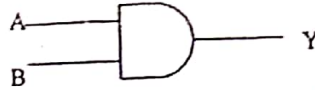

Step2 Equation

$$Y = A \cdot B$$


[Read A anded with B]

Step3 Truth table

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

d) NOR Gate

Step1 Symbol

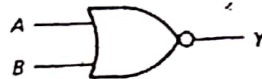

Step2 Equation

$$Y = \overline{A + B}$$

Step3 Truth Table

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

e) NAND Gate

Step1 Symbol



Step2 Equation


$$Y = \overline{A \cdot B}$$

Step3 Truth Table

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

f) XOR Gate

Step1 Symbol

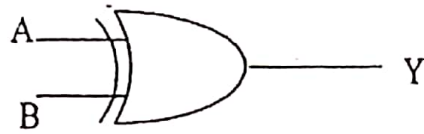

Step2

Step3

$$Y = \bar{A}.B + A.\bar{B}$$

Truth Table

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Differs from OR Gate only because of last step.

g) X - NOR Gate

Step1 Symbol



Step2 Equation

$$Y = A.\bar{B} + \bar{A}.B$$


Step3 Truth Table

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

Important Theorems

1. De Morgan's first theorem

a)

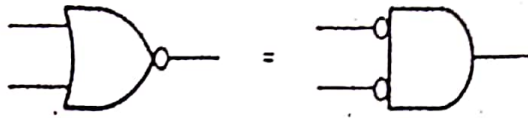

b)

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$

c)

Truth Table


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Truth Table

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

2) De Morgan's second theorem

a)

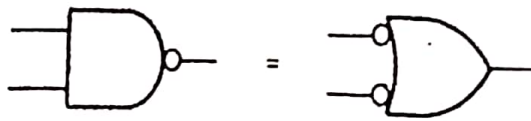

b)

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

c)

Truth Table


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

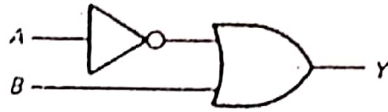PROBLEMS – LOGIC GATES

Pr.1) Write equation and make truth table of given circuit.




Solution:-

Equation $Y = \bar{A} + B$

Truth Table

A	B	$Y = \bar{A} + B$
0	0	1
0	1	1
1	0	0
1	1	1

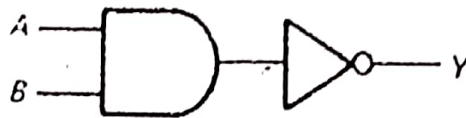Pr.2) Write equation and make truth table of given circuit.




Solution:-

Equation $Y = \overline{A.B}$

Truth Table

A	B	$Y = \overline{A.B}$
0	0	1
0	1	1
1	0	1
1	1	0

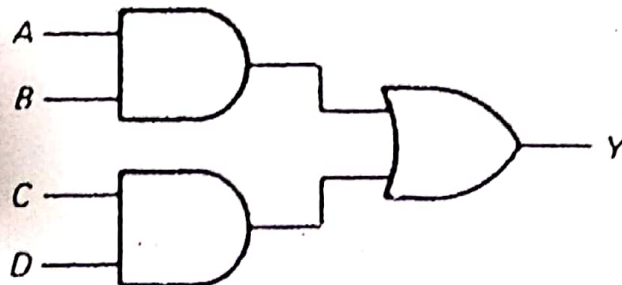Pr.3) Write equation and make truth table of given circuit.




Solution:

Equation $Y = AB + CD$

Truth Table

A	B	C	D	Y = AB + CD
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

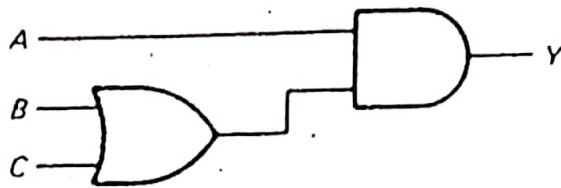Pr.4) Write equation and make truth table of given circuit.




Solution:

Equation $Y = A(B + C)$

Truth Table

A	B	C	Y=A(B+C)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

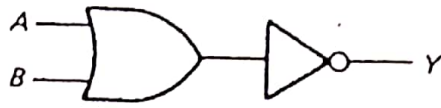Pr.5) Write equation and make truth table of given circuit.



Solution:

Equation $Y = \overline{(A + B)}$

Truth Table

A	B	$Y = \overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

Pr.6) Write equation and make truth table of given circuit.




Solution:

Equation $Y = \overline{(A + B + C)}$

Truth Table

A	B	C	$Y = \overline{A + B + C}$
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

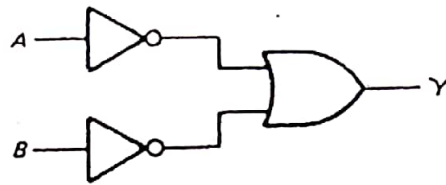Pr.7) Write equation and make truth table of given circuit.




Solution:

Equation $Y = \bar{A} + \bar{B}$

Truth Table

A	B	$Y = \bar{A} + \bar{B}$
0	0	1
0	1	1
1	0	1
1	1	0

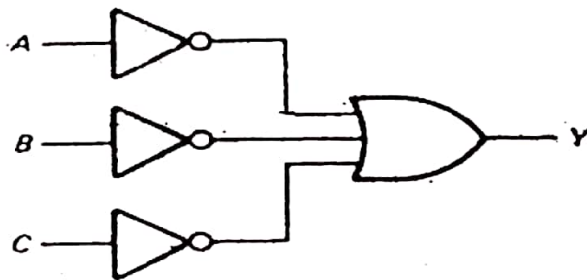Pr.8) Write equation and make truth table of given circuit.




Solution

Equation $Y = \bar{A} + \bar{B} + \bar{C}$

Truth Table

A	B	C	$Y = \bar{A} + \bar{B} + \bar{C}$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Pr.9 Write equation of given circuit.

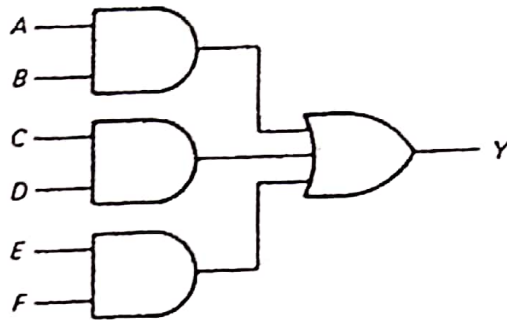


Solution:

Equation

$$Y = AB + CD + EF$$

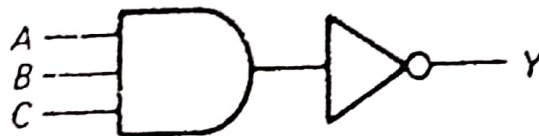Pr.10 Write equation and make truth table of given circuit.



Solution:


Equation

$$Y = \overline{A.B.C}$$

Truth table

A	B	C	$Y = \overline{A.B.C}$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

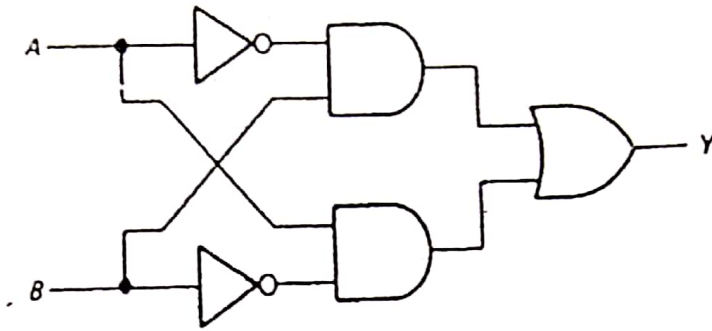Pr.11 Write equation and make truth table of given circuit.



Solution:


Equation $\bar{A}.B + \bar{B}.A$

It is XOR gate circuit

Truth Table

A	B	$Y = \bar{A}.B + \bar{B}.A$
0	0	0
0	1	1
1	0	1
1	1	0

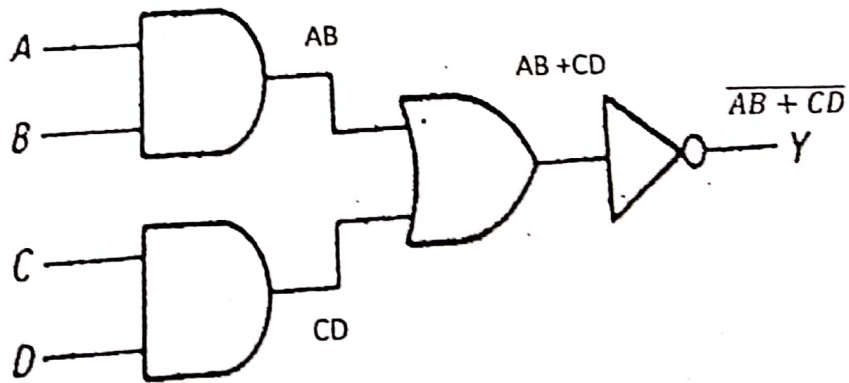Pr.12 Write equation and make truth table of given circuit.




Solution:

Equation $Y = \overline{AB + CD}$

Truth Table

A	B	C	D	$Y = AB + CD$
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

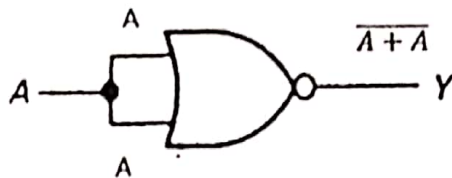Pr.13 Write equation and make truth table of given circuit.




Solution:

Equation $Y = \overline{A + A}$

Truth Table

A	$Y = \overline{A + A}$
0	1
1	0

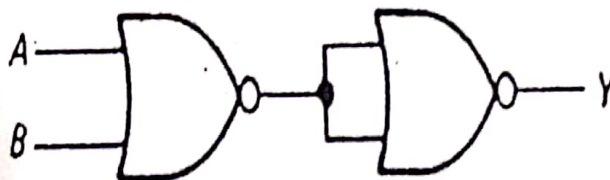Pr.14 Write equation and make truth table of given circuit.




Solution:

Equation $Y = A + B$

Truth Table

A	B	Y = A+B
0	0	0
0	1	1
1	0	1
1	1	1

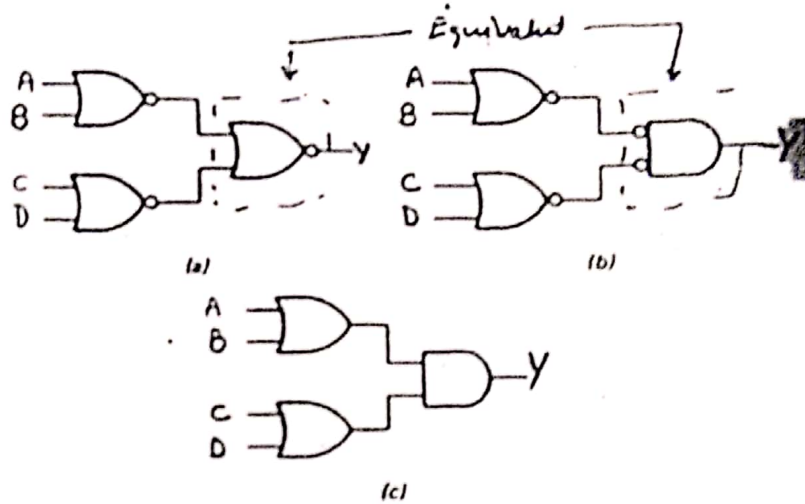Pr.15 Write equation and make truth table of given circuit.



Solution:


Equation: $Y = (A + B) (C + D)$

There are $2^4 = 16$ words in Truth Table

Truth Table

A	B	C	D	Y = (A + B) (C + D)
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

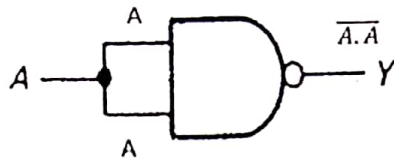Pr.16 Write equation and make truth table of given circuit.




Solution:

Equation $Y = \overline{A.A}$

Truth Table

A	$Y = \overline{A.A}$
0	1
1	0

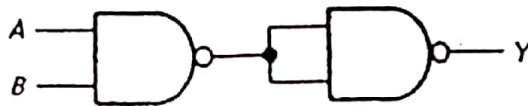Pr.17 Write equation and make truth table of given circuit.




Solution

Equation $Y = AB$

Truth Table

A	B	$Y = AB$
0	0	0
0	1	0
1	0	0
1	1	1

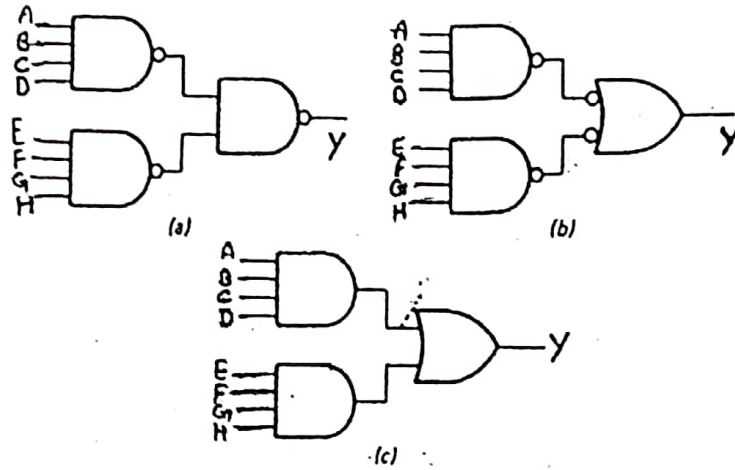Pr.18 Write equation and make truth table of given circuit.



Solution

Equation $Y = (ABCD) + (EFGH)$

Truth Table has $2^8 = 256$ words.

Important Board Questions


Q1. What is Integrated circuit?

Ans. Integrated circuit is that circuit in which the circuit components such as resistors, capacitors, diodes and transistors etc are automatically parts of a small semiconductor chip.


Q2. Make AND gate by using NOR gate.

Solution:


Step1

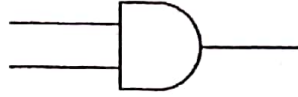


Step2

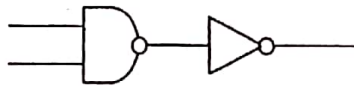


Step3

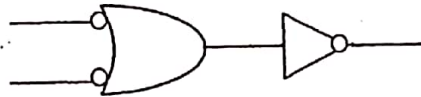

Step4

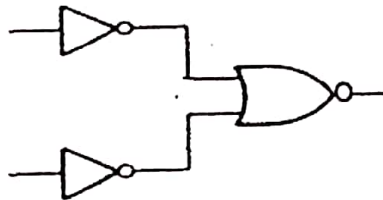


Step5

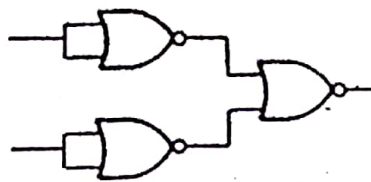

Q3. Make AND gate by using NAND gate.


Step1

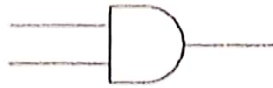

Step2




Step3

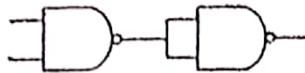

Q4. Make OR gate by using NAND gate


Step1

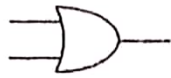


Step2




Step3

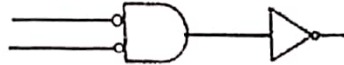


Step4

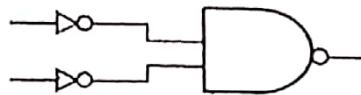

Step5

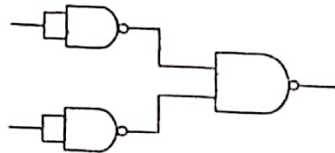


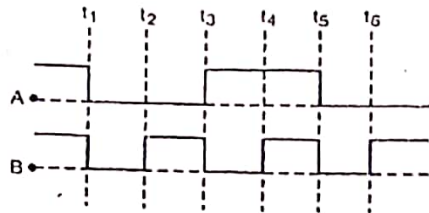Q5. Sketch the output y from a NAND gate having inputs A and B given below.




Sol. For NAND gate the Boolean expression is $y = \overline{A \cdot B}$
 For the given wave form, we have the following values for A, B and y.

A	B	Y
1	1	0
0	0	1
0	1	1
1	0	1
1	1	0
0	0	1
0	1	1

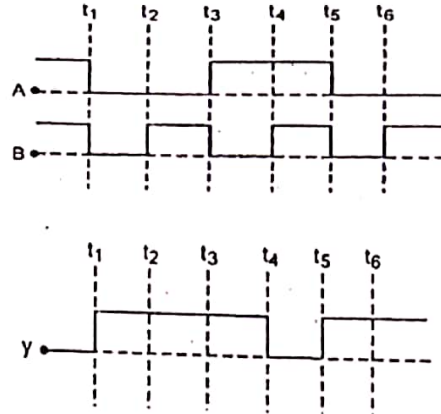

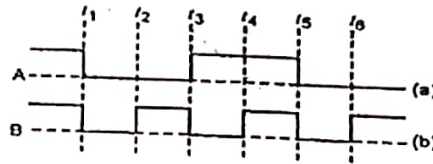Q6. Sketch the output y from a NOR gate having inputs A and B as given in Fig.



Sol. For NOR gate the Boolean expression is $y = \overline{A + B}$
 For the given wave form, we have the following values for A, B and y.

A	B	Y
1	1	0
0	0	1
0	1	0
1	0	0
1	1	0
0	0	1
0	1	0

