

# *Physics Notes*

BY

**Er. Lalit Sharma**

B.Tech (Electrical)

Ex. Lecturer Govt. Engg. College Bathinda

Physics Faculty Ranker's Point, Bathinda

**Arun Garg**

M.Sc. Physics

Gold Medalist

Physics Faculty Ranker's Point, Bathinda

**Class:10+2**

**Unit: IV**

**Topic: Electromagnetic Induction & Alternating Currents**

**SYLLABUS: UNIT-IV-B**

Electromagnetic induction; Faraday's law, induced emf and current; Lenz's Law; Eddy currents, Self and mutual inductance.

Need for displacement current.

Alternating current, peak and rms value of alternating current/voltage; reactance and impedance; LC oscillations (Qualitative treatment only), LCR series circuit, resonance; power in AC circuits, wattles current.

AC generator and transformer.






All rights reserved. No part of this publication may be reproduced, stored in a retrieval system, or transmitted in any form or by any means, electronic, mechanical, photocopying, recording, or otherwise without the prior written permission of the publishers.

Q.No.	Topic/Question	Page No.
	<u>Unit-IV-B</u>	
1.	Derive an expression for “Average value” of alternating current (sine wave) a) Half wave b) Full wave.	1
2.	Derive an expression for “RMS” value of alternating current (sine wave) a) Half wave b) Full wave.	3
3.	Find magnitude and phase of current in pure resistive (R) circuit when sine voltage is applied across it?	5
4.	Find magnitude and phase of current in pure induction (L) circuit when sine voltage is applied across it.	7
5.	Find magnitude and phase of current in pure capacitor circuit when sine voltage is applied across it.	9
6.	Find magnitude and phase of current in R-L series circuit when sine voltage is applied across it.	11
7.	Find magnitude and phase of current in R-C series circuit when sine voltage is applied across it.	15
8.	Find magnitude and phase of current in R-L-C series circuit when sine voltage is applied across it.	17
9.	What is “Resonance” in R-L-C circuit? Derive expression for resonant frequency?	19
10.	a) Prove Energy stored in an inductor is $\frac{1}{2} \cdot L \cdot I^2$ ? b) Prove Energy density in magnetic field is $\frac{1}{2} \cdot \mu \cdot H^2$ ?	21
11.	Find Power associated with a “Resistor” in a.c. ?	23
12.	Find Power associated with an “Inductor” in a.c.?	25
13.	Find Power associated with a “Capacitor” in a.c. ?	27
14.	Prove $P = V_{rms} I_{rms} \cos \phi$ , where $\phi$ is phase difference between voltage and current?	29
15.	What is an L-C oscillator? Derive expression for resonant frequency of L-C oscillator?	31
16.	What do you mean by Quantity factor of a circuit? Explain.	31
17.	Discuss Construction, Working and Efficiency of a transformer.	33
18.	Discuss Construction, Working of A.C. Generator.	35


Q.1. Derive an expression for "Average value" of alternating current (sine wave)

- Half wave
- Full wave.

Ans.a) **Half wave**

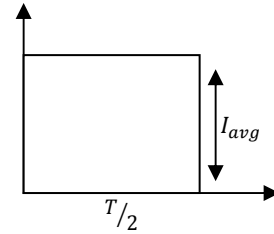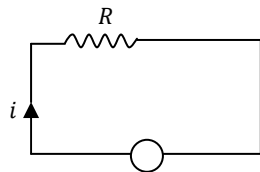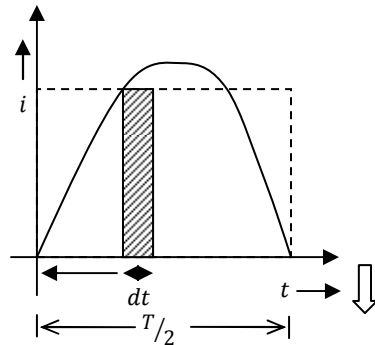

$$I_{avg} = \frac{2}{\pi} I_{max}$$

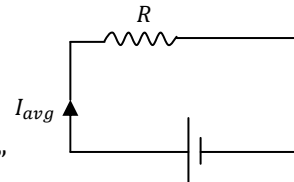

- Average value of current is defined on the basis of "Charge" flowing in a circuit.
- Average flowing value of current in a circuit is that a.c which when flowing in a circuit allow same charge to flow as is flowing in a.c. current.

$$\int_0^{T/2} i dt = I_{avg} \left( \frac{T}{2} \right)$$

$$\int_0^{T/2} I_m \sin \omega t dt = I_{avg} \left( \frac{T}{2} \right)$$


$$I_m \left[ -\frac{\cos \omega t}{\omega} \right]_{t=0}^{t=\frac{T}{2}} = I_{avg} \left( \frac{T}{2} \right) \quad \left[ \omega = \frac{2\pi}{T} \right]$$

$$\frac{I_m}{\omega} \left[ -\frac{\cos 2\pi}{\omega} \times \frac{T}{2} - (-\cos 0) \right] = I_{avg} \left( \frac{T}{2} \right)$$

$$\frac{I_m}{\omega} (2) = I_{avg} \left( \frac{T}{2} \right)$$

$$I_{avg} = \frac{2}{\pi} I_{max}$$

$$I_{avg} = 0.64 I_{max}$$

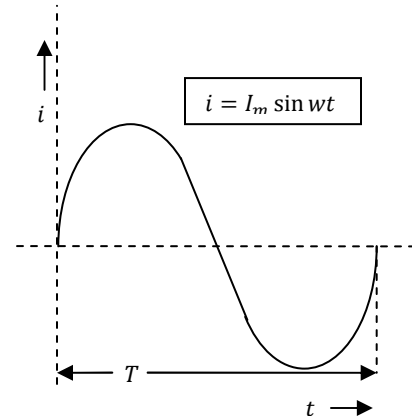

b) **Full wave:**  $I_{avg} \cdot T$

$$= \int_0^T I_m \sin \omega t dt = 0 \text{ so,}$$

$$I_{avg} = 0$$

**Q2. Derive an expression for “RMS” value of alternating current (sine wave)**

- Half wave
- Full wave.

Ans.

- RMS value is defined on the basis of “Heating effect”.

RMS value is that *dc* current which when flowing in a resistance gives same heating effect as given by alternating current.

$$\begin{aligned}
 I_{rms}^2 \cdot R \cdot \frac{T}{2} &= \int_0^{T/2} i^2 R \cdot dt \\
 I_{rms}^2 \cdot 1 \cdot \frac{T}{2} &= \int_0^{T/2} i^2 dt \\
 &= \int_0^{T/2} I_{max}^2 \sin^2 \omega t dt \\
 &= \int_0^{T/2} I_{max}^2 \left( \frac{1 - \cos 2\omega t}{2} \right) dt \\
 &= I_{max}^2 \cdot \frac{1}{2} \left[ t - \frac{\sin 2\omega t}{2\omega} \right]_0^{T/2} \\
 &= I_{max}^2 \cdot \frac{1}{2} \left[ \frac{T}{2} - \frac{\sin 2 \left( \frac{2\pi}{T} \right) \times \frac{T}{2}}{2\omega} \right] - [0 - \sin 0] \\
 &= I_{max}^2 \cdot \frac{1}{2} \left[ \frac{T}{2} - 0 \right] \\
 I_{rms}^2 \cdot 1 \cdot \frac{T}{2} &= \frac{I_{max}^2}{2} \cdot \frac{T}{2}
 \end{aligned}$$

$$\boxed{I_{rms} = \frac{I_{max}}{\sqrt{2}}}$$


FORM FACTOR:

$$= \frac{I_{rms}}{I_{avg}} \quad (\text{Ratio of r.m.s value to avg. value})$$

$$= \frac{\frac{I_{max}}{\sqrt{2}}}{\frac{2}{\pi} I_{max}}$$

$$= \frac{\pi}{2\sqrt{2}}$$

$$= 1.11$$

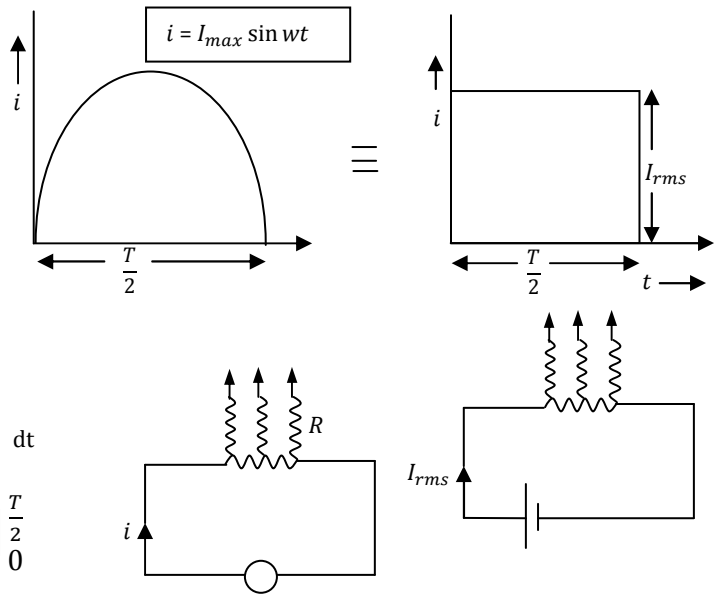


**Q3. Find magnitude and phase of current in pure resistive (R) circuit when sine voltage is applied across it?**

Ans.

Step 1:-

Draw 2 figures i.e. (Fig. I, II)

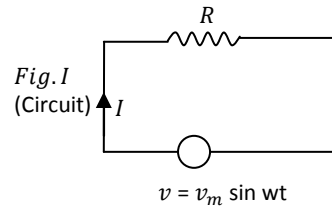

Step 2:-


Write relationship between  $i$  and  $v$

$$v = R i$$

$$i = \frac{v}{R}$$


$$i = \left(\frac{V_m}{R}\right) \sin \omega t$$

$i$	$= I_{max} \sin \omega t$
-----	---------------------------

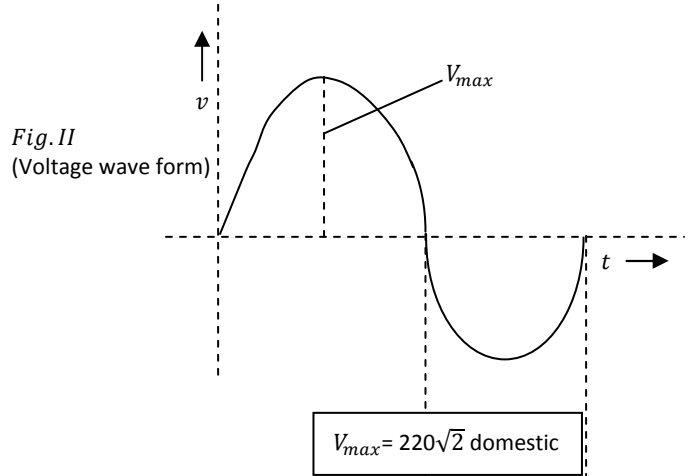

where  $I_{max} = \frac{V_m}{R}$


Draw current wave form

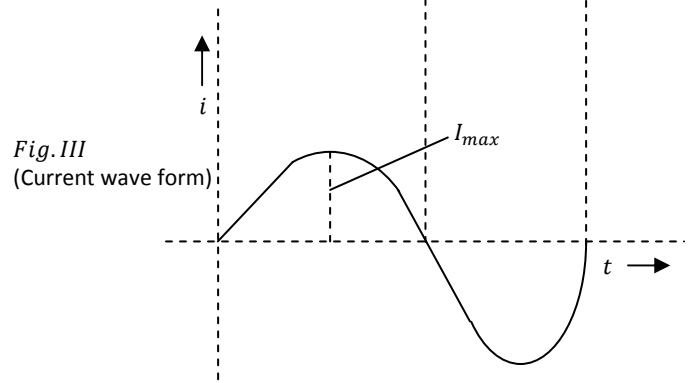

Step 3:-

After analyzing voltage and current wave form, Draw "Phasor" diagram.

$\bar{V}$  and  $\bar{I}$  are in phase.

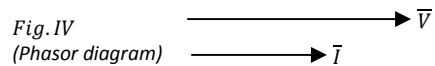


**Q4. Find magnitude and phase of current in pure induction (L) circuit when sine voltage is applied across it.**

Ans.

Step 1:-

Draw 2 figures i.e. (Fig. I, II)

$$v = V_m \sin \omega t$$

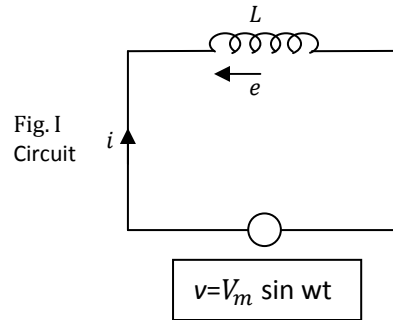

Step 2:-


Write relationship between  $i$  and  $v$

$$v = -e$$

$$v = -(-L \frac{di}{dt})$$

$$v = L \frac{di}{dt}$$

$$di = \frac{v}{L} dt$$

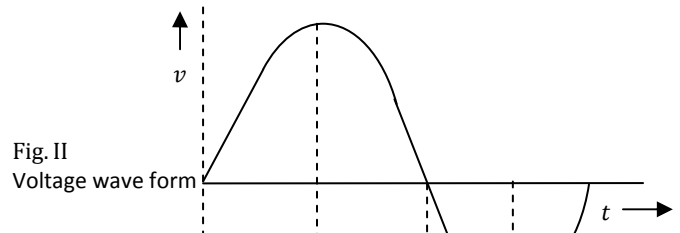

Integrating both sides


$$\int di = \int \left( \frac{V_m}{L} \sin \omega t \right) dt$$

$$i = \frac{V_m}{L} \left( -\frac{\cos \omega t}{\omega} \right)$$

$$i = \frac{V_m}{L\omega} \left[ \sin \left( \omega t - \frac{\pi}{2} \right) \right]$$

$$i = I_{max} \sin \left( \omega t - \frac{\pi}{2} \right)$$

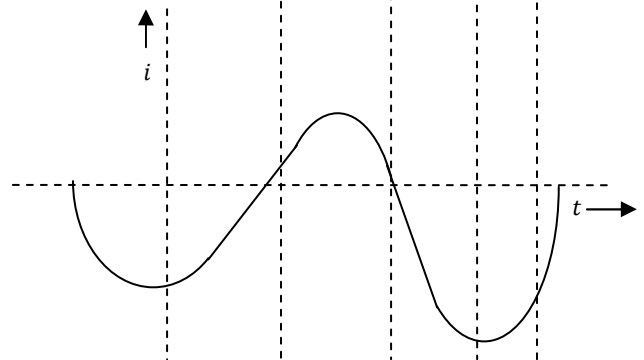
$$\left\{ \text{where } I_{max} = \frac{V_m}{L\omega} = \frac{V_m}{X_L} \leftarrow \text{Inductive reactance} \right\}$$



Step 3:-

Phasor diagram

Current lags voltage by  $\frac{\pi}{2}$

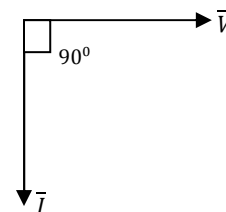

**Q5. Find magnitude and phase of current in pure capacitor circuit when sine voltage is applied across it.**

Current leads by  $\frac{\pi}{2}$  in a pure capacitor.


Ans.

Step 1:-

Draw 2 figures i.e. (Fig. I, II)

$$v = V_m \sin \omega t$$

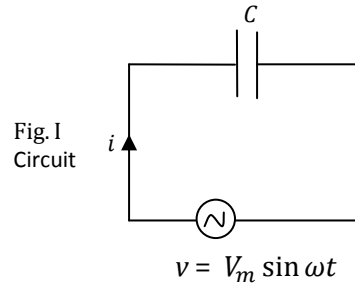The above voltage is applied across a capacitor.



Step 2:-


Write relationship between  $i$  and  $v$

$$\begin{aligned} i &= \frac{dq}{dt} \\ i &= \frac{d(Cv)}{dt} \\ i &= C \frac{dv}{dt} = C \frac{d(V_m \sin \omega t)}{dt} \\ i &= C V_m (\cos \omega t) \cdot \omega \\ &= (C V_m \cdot \omega) \cos \omega t \\ &= \frac{V_m}{\frac{1}{C\omega}} \cdot \cos \omega t \\ &= \frac{V_m}{X_C} \cdot \cos \omega t \end{aligned}$$

$$\begin{aligned} i &= I_m \cos \omega t \\ &= I_m \left[ \sin \left( \omega t + \frac{\pi}{2} \right) \right] \end{aligned}$$

$$X_C = \frac{1}{C\omega} \text{ is capacitive reactance}$$


Fig. II  
Voltage wave form

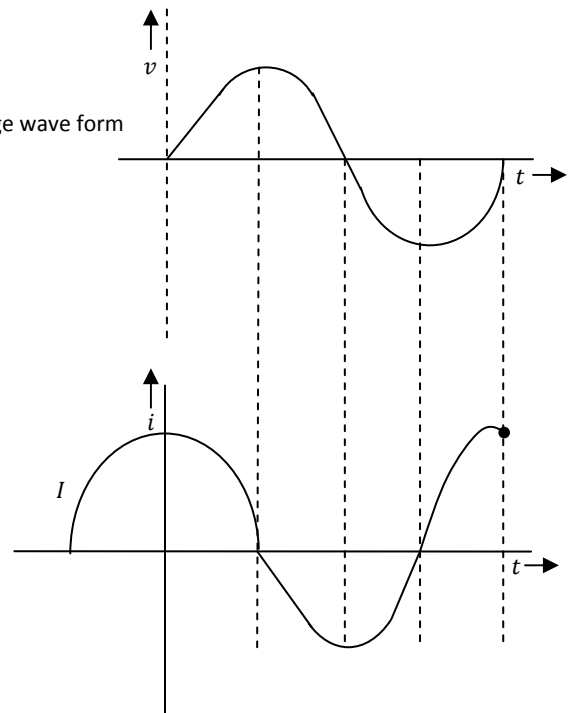

Step 3:-

$$v = V_m \sin \omega t$$
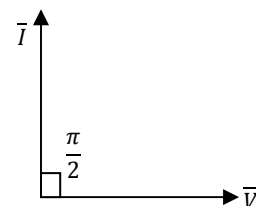
$$i = I_m \sin \left( \omega t + \frac{\pi}{2} \right)$$




**Q6. Find magnitude and phase of current in R-L series circuit when sine voltage is applied across it.**

Ans.

Step 1:-

Draw circuit diagram

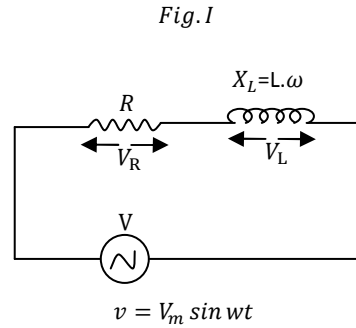


Step 2:-

Mark voltages, currents in circuit diagram.


Step 3:-

Draw phasor diagram for voltages

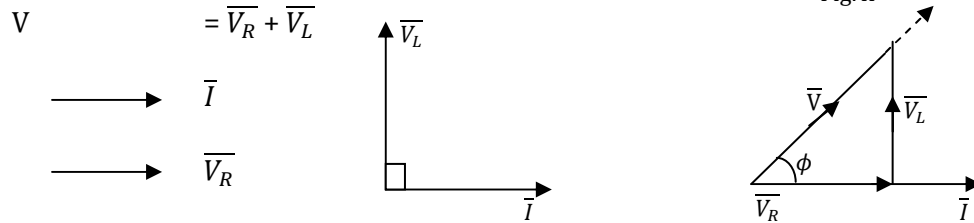

Step 4:-

Draw Impedance triangle

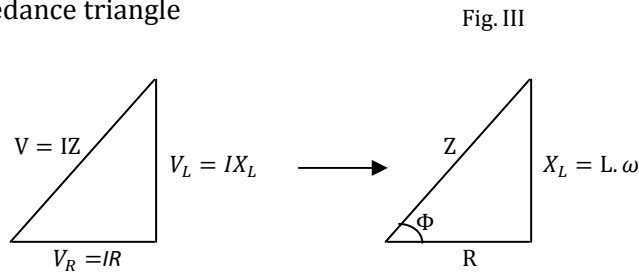


Impedance,  $Z = \sqrt{R^2 + X_L^2}$

Step 5:-

Draw voltage and current wave form

Current lags voltage by  $\Phi$

$I = \frac{V}{Z}$

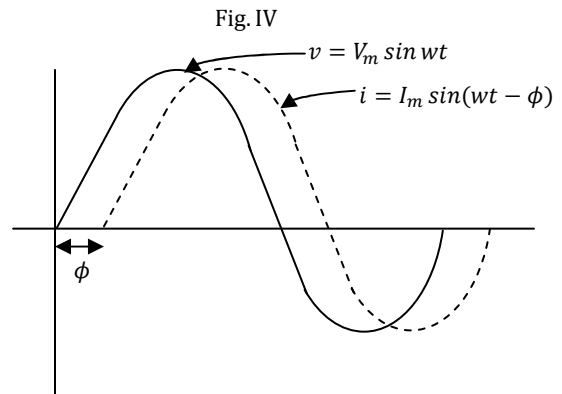



## Discussion for Q.6

$$\begin{aligned}
 1. \text{ If } L = 0, \quad Z &= \sqrt{R^2 + (L\omega)^2} \\
 &= \sqrt{R^2 + 0} \\
 &= \sqrt{R^2}
 \end{aligned}$$

$$Z = R$$

Pure resistive network

$$\Phi = 0$$

$\bar{V}$  and  $\bar{I}$  are in phase

$$\begin{aligned}
 2. \text{ If } R = 0, \quad Z &= \sqrt{R^2 + (L\omega)^2} \\
 &= \sqrt{0 + (L\omega)^2}
 \end{aligned}$$



$$Z = L\omega$$

$$Z = X_L \quad [X_L = L\omega]$$

Pure inductive network

$$\Phi = 90^\circ$$

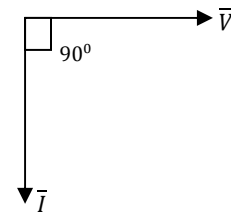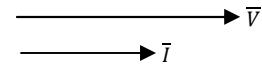Current lags voltage by  $\frac{\pi}{2}$ .




**Q7. Find magnitude and phase of current in R-C series circuit when sine voltage is applied across it.**

Fig. I

Ans.

Step 1:-

Draw circuit diagram

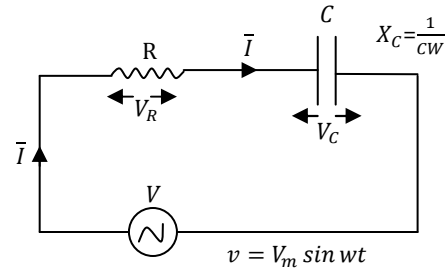

Step 2:-


Mark voltages, currents in circuit diagram.

Step 3:-

Draw phasor diagram for voltages


$$\bar{V} = \bar{V}_R + \bar{V}_C$$

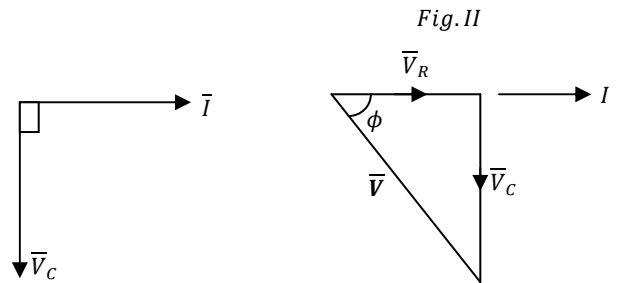$\longrightarrow \bar{I}$  and  
 $\longrightarrow \bar{V}_R$



Step 4:-

Draw Impedance triangle

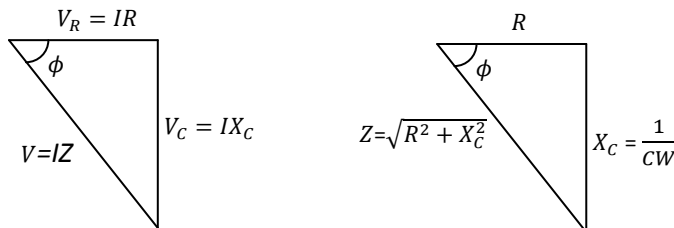



Impedance,  $Z = \sqrt{R^2 + X_C^2}$

Step 5:-

Draw voltage and current wave form

Current leads voltage by  $\Phi$

Fig. IV

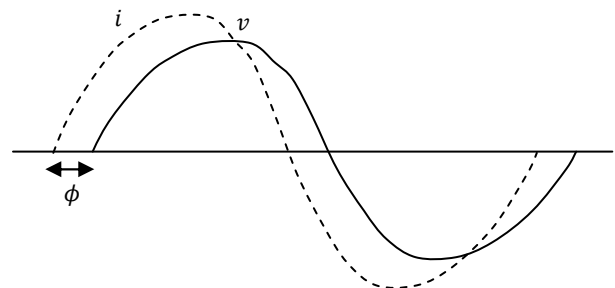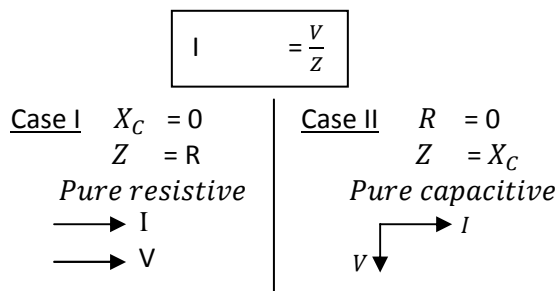


**Q8. Find magnitude and phase of current in R-L-C series circuit when sine voltage is applied across it.**

Ans.

Step 1:-

Draw circuit diagram

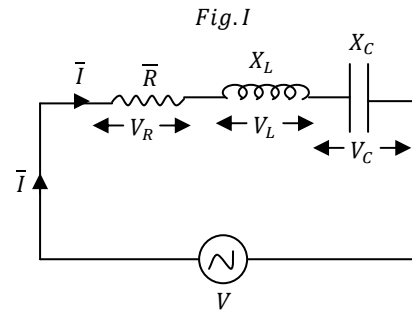

Step 2:-


Mark voltages, currents in circuit diagram.

Step 3:-

Draw phasor diagram for voltages


$$\bar{V} = \bar{V}_R + \bar{V}_C + \bar{V}_L$$

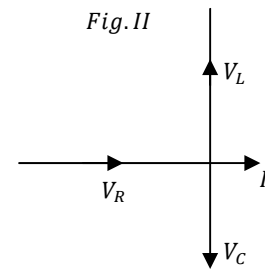Inductive effect is more than capacitive effect. (Assumption)




Step 4:-

Draw Impedance triangle

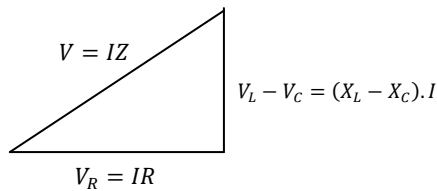

Impedance, Z	$= \sqrt{R^2 + (X_L - X_C)^2}$
--------------	--------------------------------

Fig. III

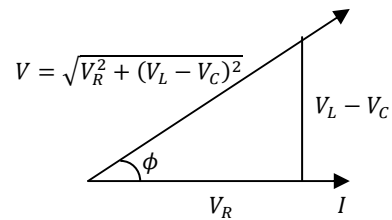

Step 5:-

Draw voltage and current wave form

$I$	$= \frac{V}{Z}$
-----	-----------------

Current lags voltage by  $\Phi$


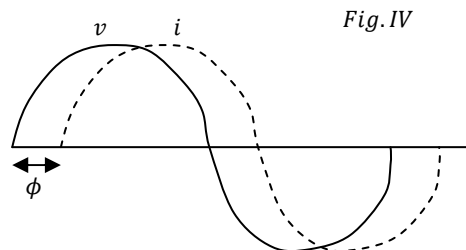
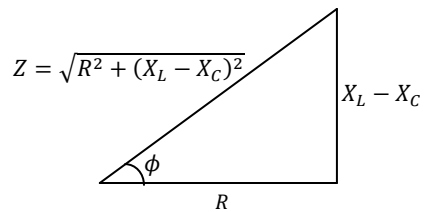


Fig. IV

**Q9. What is "Resonance" in R-L-C circuit? Derive expression for resonant frequency?**

Ans.

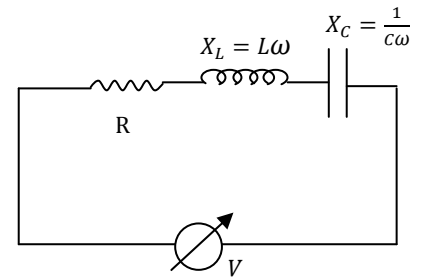- a) Resonance in R-L-C circuit means condition when current is optimum.  
That is for series R-L-C circuit, current is maximum.



- b-1) As  $\omega$  changes,  $X_L = L\omega$  and  $X_C = \frac{1}{c\omega}$  change

$$Z = \sqrt{R^2 + \left(L\omega - \frac{1}{c\omega}\right)^2}$$

$$Z_{min} = R$$



When  $L\omega_0 = \frac{1}{c\omega_0}$

$$\omega_0^2 = \frac{1}{LC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$2\pi f_0 = \frac{1}{\sqrt{LC}}$$

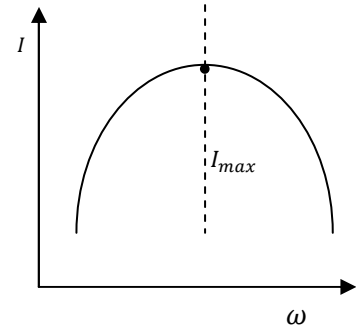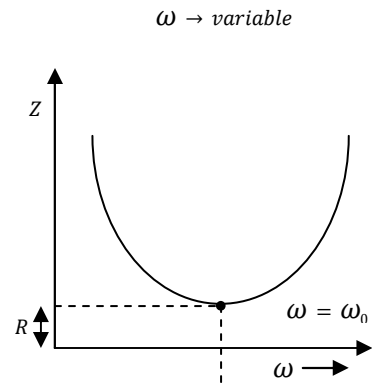
$f_0 = \frac{1}{2\pi\sqrt{LC}}$
---------------------------------



- b-2) When  $f_0 = \frac{1}{2\pi\sqrt{LC}}$


current is maximum.

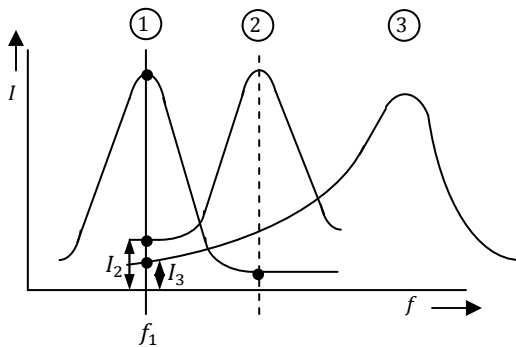- b-3) Three station frequency is fed in transistor circuit.  
Sharpness of resonance curve should be high



$I_2$  and  $I_3$  are currents due to station 2 and 3 when station 1 is tuned at frequency  $f_1$

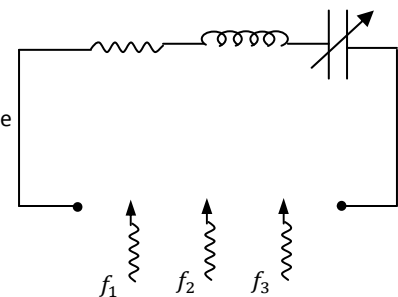Sharpness of resonance curve should be high




- Q10. a) Prove Energy stored in an inductor is  $\frac{1}{2} \cdot L \cdot I^2$  ?**  
**b) Prove Energy density in magnetic field is  $\frac{1}{2} \cdot \mu \cdot H^2$  ?**

Ans.a) Energy is stored in an inductor in form of magnetic field.

When current increases from  $I$  to  $I + dI$ , flux linking increase.


Rate of change of flux causes an emf  $e$  as shown in diagram.

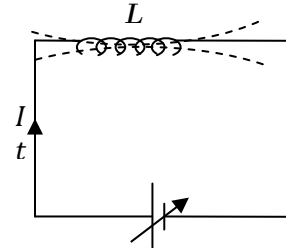Battery does work against  $e$  and energy supplied by battery gets stored in inductor in form of magnetic field.



$$\begin{aligned} dw &= e dq \\ &= e Idt \\ w &= \int e I dt \\ &= \int L \frac{dI}{dt} \cdot I \cdot dt \\ &= L \int I dI \\ &= L \left[ \frac{I^2}{2} \right]_0^{I_0} \end{aligned}$$

$$|e| = L \frac{dI}{dt}$$

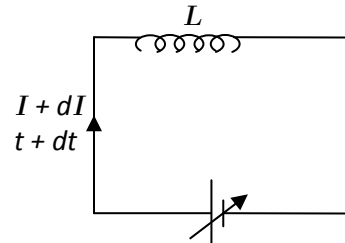


$$\text{Energy stored} = \frac{L}{2} I_0^2$$

$$\text{Energy stored} = \frac{1}{2} LI_0^2$$

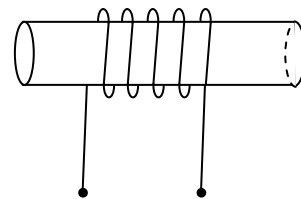b) Energy Density:

$$\begin{aligned} \text{Energy Density} &= \frac{\text{Energy}}{\text{Volume}} \\ &= \frac{\frac{1}{2} \cdot L \cdot I^2}{A \cdot l} \\ &= \frac{1}{2} \cdot \frac{\frac{N^2}{R_e} \cdot I^2}{A \cdot l} \\ &= \frac{1}{2} \cdot \frac{N^2}{R_e} \cdot \frac{I^2}{A \cdot l} \\ &= \frac{1}{2} \cdot \frac{N^2}{\frac{l}{\mu \cdot A}} \cdot \frac{I^2}{A \cdot l} \\ &= \frac{1}{2} \cdot \mu \cdot \left( \frac{N \cdot I}{l} \right)^2 \end{aligned}$$



Where  $R_e = \frac{l}{\mu \cdot A}$  is reluctance of magnetic material

$$\begin{aligned} \text{Energy Density} &= \frac{1}{2} \cdot \mu \cdot H^2 \\ \text{OR} &\quad \frac{1}{2} \cdot \frac{B^2}{\mu} \end{aligned}$$

**Q11. Find Power associated with a “Resistor” in a.c. ?**

Ans.  $dE = vi \cdot dt$

$$E = \int vi \cdot dt$$

$$= \int V_m \sin wt \cdot I_m \sin wt \cdot dt$$

$$= V_m I_m \int \sin^2 wt \cdot dt$$

$$= V_m I_m \int \frac{1 - \cos 2wt}{2} \cdot dt$$

$$= \frac{V_m I_m}{2} \left[ t - \frac{\sin 2wt}{2w} \right]_{t=0}^{t=T}$$

*Fig. II*  
(Voltage wave form)

$$= \frac{V_m I_m}{2} \left[ \left( T - \frac{\sin 2wT}{2w} \right) - \left( 0 - \frac{\sin 2w(0)}{2w} \right) \right]$$




$$= \frac{V_m I_m}{2} \left[ \left( T - \frac{\sin 2 \left( \frac{2\pi}{T} \right) (T)}{2 \left( \frac{2\pi}{T} \right)} \right) \right]$$

$$= \frac{V_m I_m}{2} \left[ \left( T - \frac{\sin 4\pi}{\frac{4\pi}{T}} \right) \right]$$

$$E = \frac{V_m I_m}{2} T$$

$$P = \frac{E}{T} = \frac{V_m I_m T}{2 T} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}}$$

$$P = V_{rms} I_{rms}$$

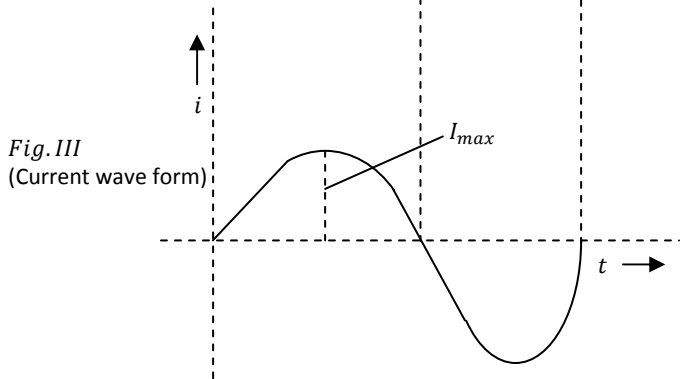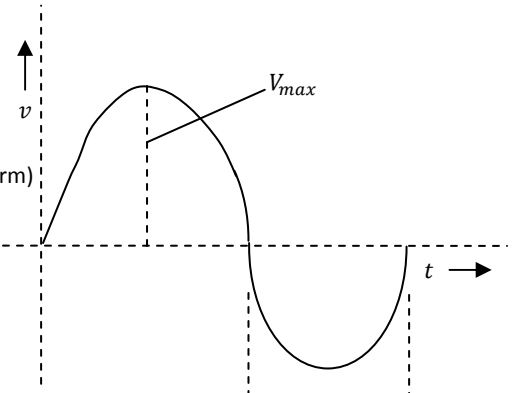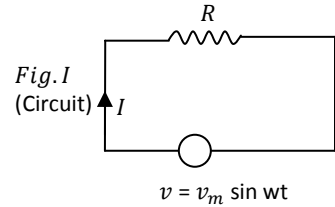

**Problem:** A voltage of 220 volt (A.C) is applied across a resistor of value 100Ω. Find reading of watt meter connected in the circuit.

**Q12. Find Power associated with an “Inductor” in a.c.?**

Ans.  $dE = vi \cdot dt$

$$E = \int vi \cdot dt$$

$$= \int V_m \sin wt \cdot I_m \sin \left( wt - \frac{\pi}{2} \right) dt$$

$$= V_m I_m \int \sin wt \sin \left( wt - \frac{\pi}{2} \right) dt$$

$$= V_m I_m \int -\sin wt \cos wt \cdot dt$$

$$= \frac{V_m I_m T}{2} \int_0^T -\sin 2wt \cdot dt$$

$$= \frac{V_m I_m}{2} \left[ \frac{\cos 2wt}{2w} \right]_{t=0}^{t=T}$$

$$= \frac{V_m I_m}{2} \left[ \left( \frac{\cos 2wt}{2w} \right) - \left( \frac{\cos 2w(0)}{2w} \right) \right]$$

$$= \frac{V_m I_m}{2} \left[ \left( \frac{\cos 2 \left( \frac{2\pi}{T} \right) T}{2 \left( \frac{2\pi}{T} \right)} - \frac{\cos 0}{\frac{2.2\pi}{T}} \right) \right]$$





$$= \frac{V_m I_m}{2} \left[ \left( \frac{\cos 4\pi}{\frac{4\pi}{T}} - 1 \right) \right]$$

$$E = \frac{V_m I_m}{2} \left[ \frac{1}{\frac{4\pi}{T}} - \frac{1}{\frac{4\pi}{T}} \right]$$

$$= 0$$

$$E = 0$$

$P$	$= 0$
-----	-------

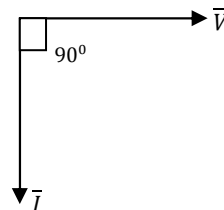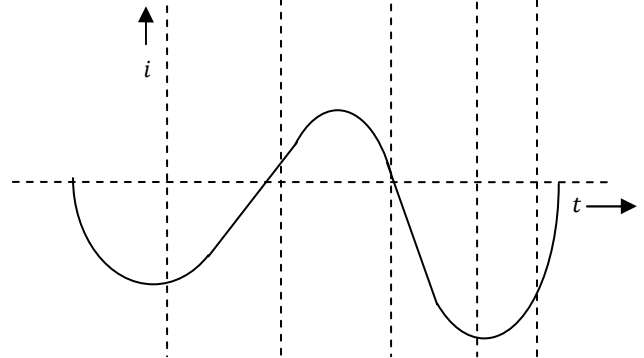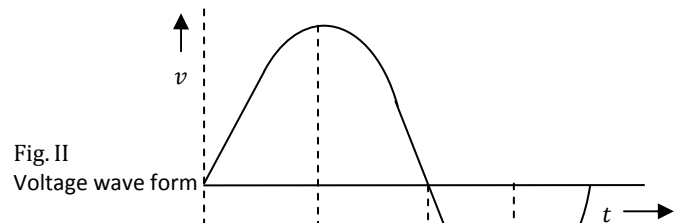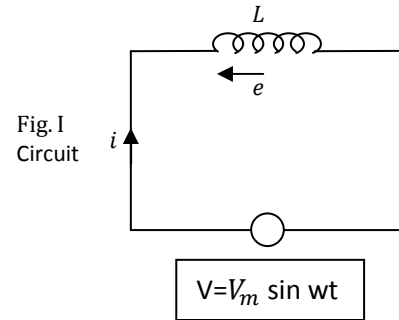

**Problem:** A voltage of 220 volt (A.C) is applied across an inductor of value 5mH. Find reading of watt meter connected in the circuit.

**Q13. Find Power associated with a "Capacitor" in a.c. ?**

Ans.  $dE = vi \cdot dt$

$$E = \int vi \cdot dt$$

$$= \int V_m \sin \omega t \cdot I_m \sin \left( \omega t + \frac{\pi}{2} \right) dt$$

$$= V_m I_m \int \sin \omega t \cdot \cos \omega t \cdot dt$$

$$= \frac{V_m I_m T}{2} \int \sin 2\omega t \cdot dt$$

$$= \frac{V_m I_m}{2} \left[ \frac{\cos 2\omega t}{2\omega} \right]_0^T$$

$$= \frac{V_m I_m}{2} \left[ \left( \frac{\cos 2\omega T}{2\omega} \right) - \left( \frac{\cos 2\omega(0)}{2\omega} \right) \right]$$

$$= \frac{V_m I_m}{2} \left[ \left( \frac{\cos 2 \frac{(2\pi)}{T} (T)}{2\omega} - \frac{\cos 0}{2\omega} \right) \right]$$

$$= 0$$

$$E = 0$$

$P = 0$
---------


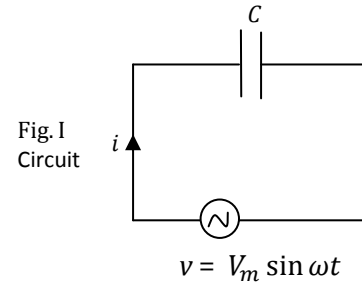


Fig. II  
Voltage wave form

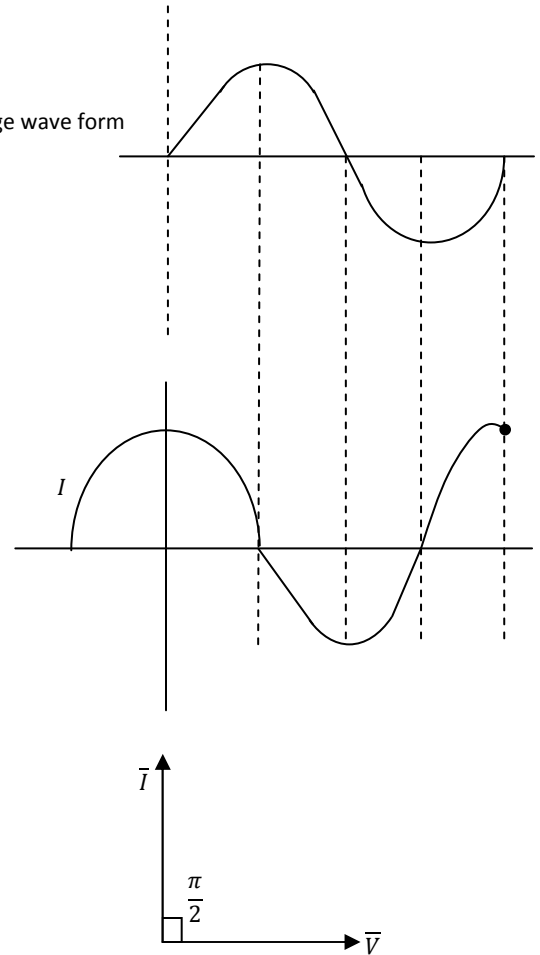

Problem: A voltage of 220 volt (A.C) is applied across a capacitor of value  $12\mu F$ . Find reading of watt meter connected in the circuit.



**Q14. Prove  $P = V_{rms} I_{rms} \cos \phi$ , where  $\phi$  is phase difference between voltage and current?**

Ans.  $dE = vi \cdot dt$

$$E = \int vi \cdot dt$$

$$= \int V_m \sin \omega t \cdot I_m \sin(\omega t - \phi) \cdot dt$$

$$= V_m I_m \int \sin \omega t \cdot \sin(\omega t - \phi) \cdot dt$$

$$= V_m I_m [(\sin \omega t) \cdot \sin(\omega t - \phi) \cdot dt]$$

$$= V_m I_m [(\sin \omega t) \cdot (\sin \omega t \cos \phi - \cos \omega t \sin \phi)] dt$$

$$= V_m I_m [\sin^2 \omega t \cos \phi dt - \sin \omega t \cos \omega t \sin \phi]$$

$$= V_m I_m \left[ (\cos \phi) \cdot \frac{T}{2} - 0 \right]$$

$$E/T = V_m I_m \left[ \cos \phi \frac{1}{2} \right]$$

$$= \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} [\cos \phi]$$

<b>P</b>	<b>= <math>V_{rms} I_{rms} \cos \phi</math></b>
----------	---

- Power factor of an A.C circuit

$$\text{Power factor} = \frac{\text{true power}}{\text{average power}}$$





$$= \cos \phi$$

$$= \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$\text{Power factor} = \cos \phi$$

$$= \frac{R}{Z} = \frac{\text{Resistance}}{\text{Impedance}}$$

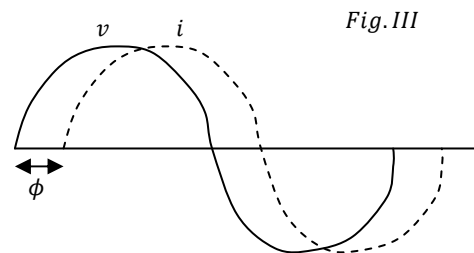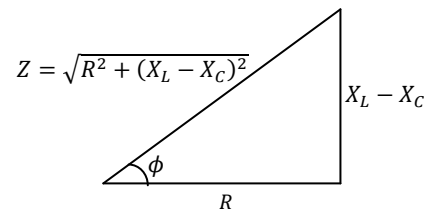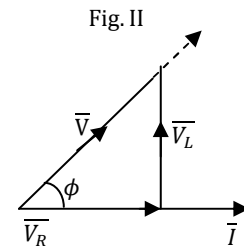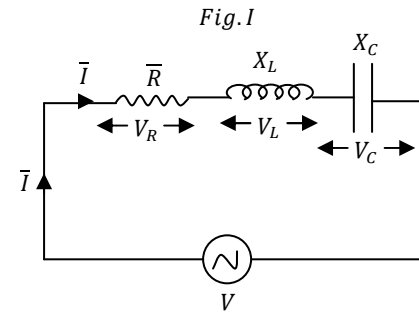Therefore, current through pure  $L$  or pure  $C$ , which consumes no power for its maintenance in the circuit is called idle current or wattless current.



**Q15. What is an L-C oscillator? Derive expression for resonant frequency of L-C oscillator?**

Ans. L-C Oscillator is a parallel combination of  $L$  and  $C$  as shown in the Fig. Energy is stored in  $L$  in form of magnetic field. Energy is stored in  $C$  in form of Electric Field. Energy keeps on oscillating from magnetic to electric and vice versa. Under resonant conditions  $I$  is zero and  $|\bar{I}_L| = |\bar{I}_C|$ .

$$\begin{aligned} \text{When } |\bar{I}_L| &= |\bar{I}_C| \\ \bar{I} &= \bar{I}_L + \bar{I}_C \\ &= 0 \end{aligned}$$

$\bar{I}$	$= \bar{I}_L + \bar{I}_C$
-----------	---------------------------

$$|I_L| = |I_C|$$

$$X_L = X_C$$


$$L\omega = \frac{1}{L\omega}$$

$$\omega^2 = \frac{1}{LC}$$


$$\omega = \frac{1}{\sqrt{LC}}$$

$$2\pi f = \frac{1}{\sqrt{LC}}$$

$$f = \frac{1}{2\pi\sqrt{LC}}$$

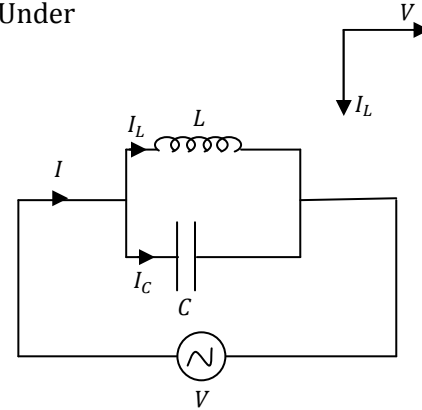

Phasor diagram

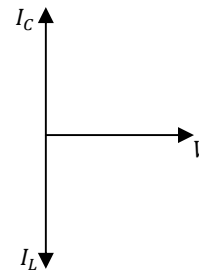

**Q16. What do you mean by Quantity factor of a circuit? Explain.**

Ans. The characteristic of series resonant circuit is determined by the  $Q$  factor or quality factor of the circuit. It defines the sharpness of tuning at resonance.

$$Q = \frac{\text{voltage across } L \text{ or } C}{\text{applied voltage (voltage across } R)}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

The difference  $w_2 - w_1 = 2\Delta w$  is called the band width of the circuit. It defines sharpness of tuning at resonance.

The values of  $Q$  usually vary from 10 to 100.

**Q17. Discuss Construction, Working and Efficiency of a transformer.**

Ans. Transformer is a device used to change A.c. voltage level/current.

Core is made up of soft iron laminations.

$$\mu_r = 1000 \text{ or more}$$

Core is in form of laminations to decrease eddy current losses/heating. Input is given to primary winding. Load is connected across secondary winding.


Number of turns of primary ( $N_1$ ) can be less than, equal to, greater than number of turns of secondary ( $N_2$ ).

Thickness of wires depends on current to be carried Primary and Secondary are co-axial for practical purpose, i.e. flux linking is max.

**Working**

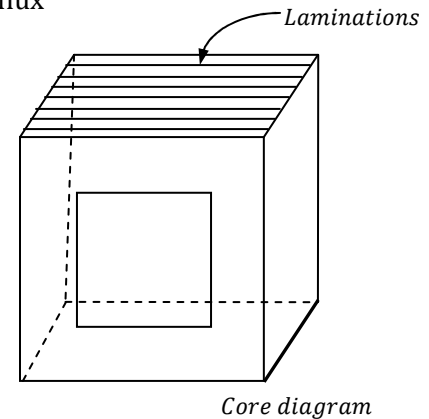(i)  $\frac{emf}{turn} = \frac{d(flux)}{dt}$  is same for all turns.

$$\frac{V_1}{N_1} = \frac{V_2}{N_2} \quad \text{--- (1)}$$



(2) Law of conservation of energy (Assumption): No losses in transformer


Input Energy = Output Energy

$$V_1 \cdot I_1 = V_2 \cdot I_2$$

$$\frac{V_1}{V_2} = \frac{I_2}{I_1} \quad \text{--- (2)}$$

From (1) and (2)
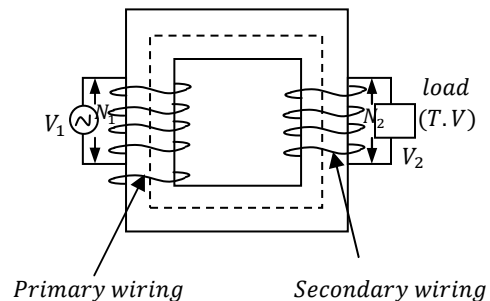
$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$



(3) Efficiency,  $\eta = \frac{\text{output}}{\text{input}} = \frac{V_2 \cdot I_2}{V_1 \cdot I_1}$

(Output = Input - Losses)

**Q18. Discuss Construction, Working of A.C. Generator.**



Ans.  $\phi = BA \cos\theta$

$$|e| = \frac{d\phi}{dt} = \frac{d}{dt} (BA \cos\theta)$$


$$= BA \frac{d}{dt} (\cos\theta) \quad (\theta = \omega t.)$$

$$= (BA \omega) \sin \omega t$$

$e = e_{max} \sin \omega t$

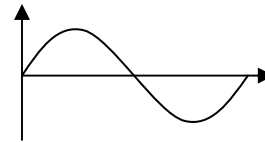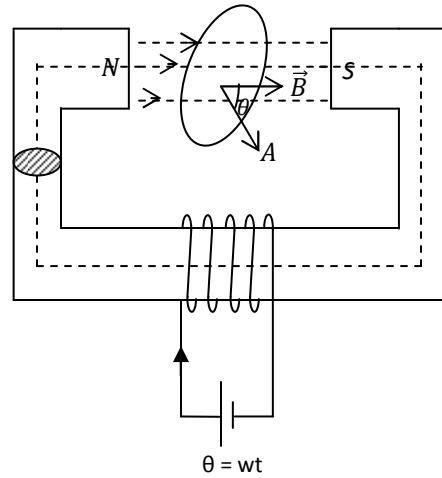

**DC Generator**

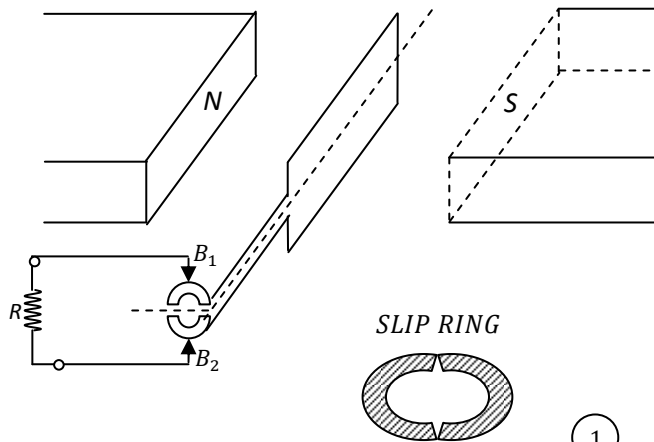

**2-D view**

